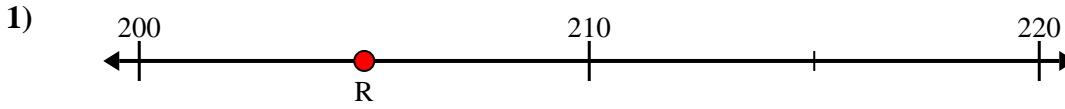





Finde den Wert von R.


Antworten



1. _____

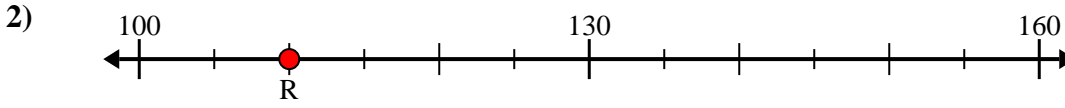


2. _____

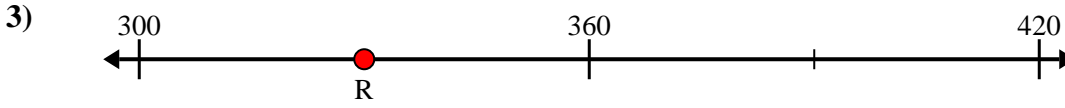


3. _____

4. _____

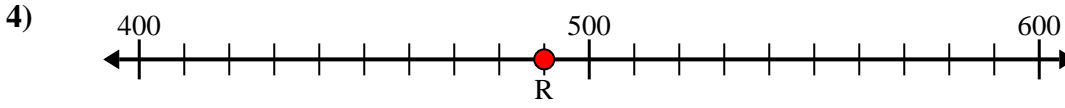


5. _____

6. _____

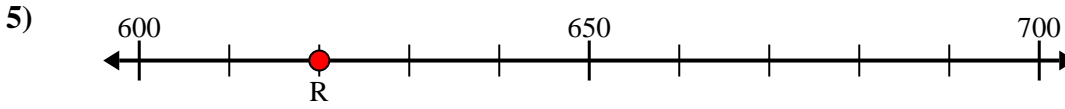





7. _____

8. _____

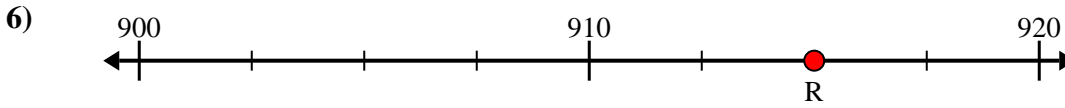

9. _____


10. _____

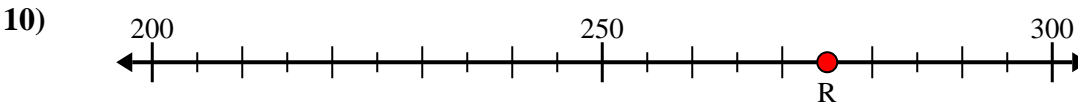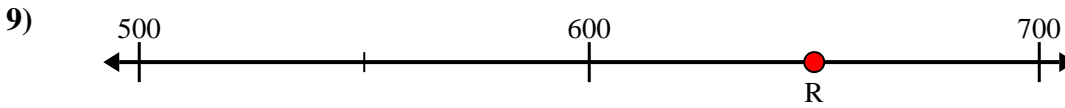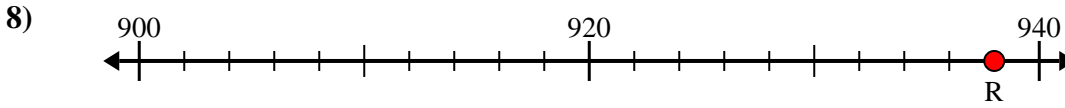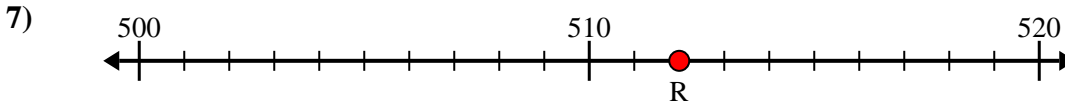




Finde den Wert von R.


Antworten

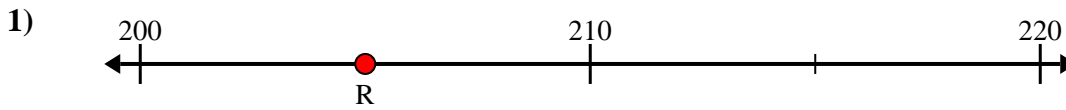

1. 205

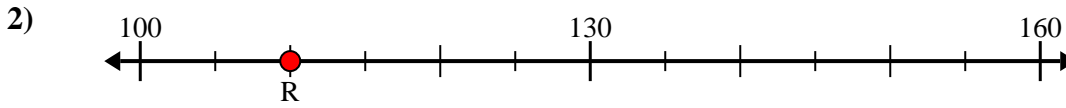


2. 110

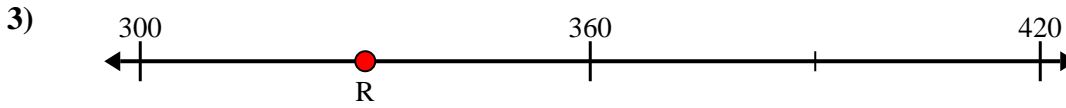


3. 330

4. 490

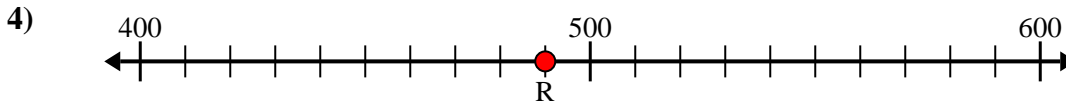


5. 620

6. 915

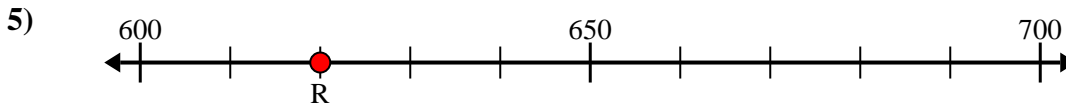

7. 512

8. 938

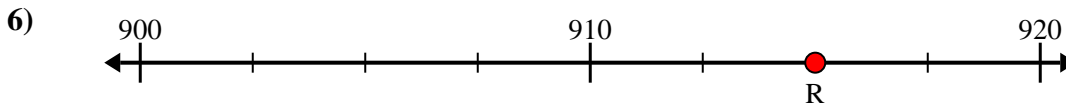

9. 650

10. 275

